



中国科学技术大学
University of Science and Technology of China

计算系统概论A
Introduction to Computing Systems
(CS1002A.03)

Chapter 3

Digital Logic Structures

陈俊仕

cjuns@ustc.edu.cn

2022 Fall

计算机科学与技术学院
School of Computer Science and Technology

Previously



■ Microprocessors contain billions of transistors

- Intel Core 2 Duo (2006)/core i7 (2015): 0.291/1.9 billion
- AMD Barcelona (2006)/Ryzen (2017): 0.463/4.8 billion
- IBM Power6: 0.79 billion

■ Transistor: Building Block of Computers

- Logically, each transistor acts as a **switch**

■ Combined to implement logic functions


- AND, OR, NOT

■ Building Functions from Logic Gates

- Combinational Logic Circuit
- Sequential Logic Circuit

Previously: Transistor


■ N-type MOS

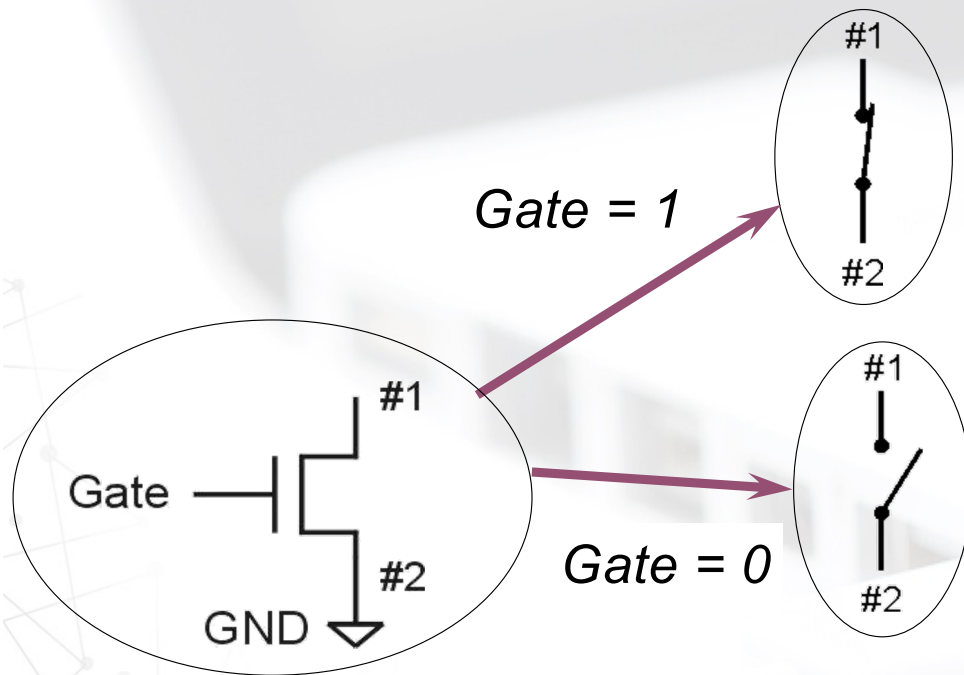

Terminal #2 must be connected to GND (0V).

2023/10/11


■ P-type MOS

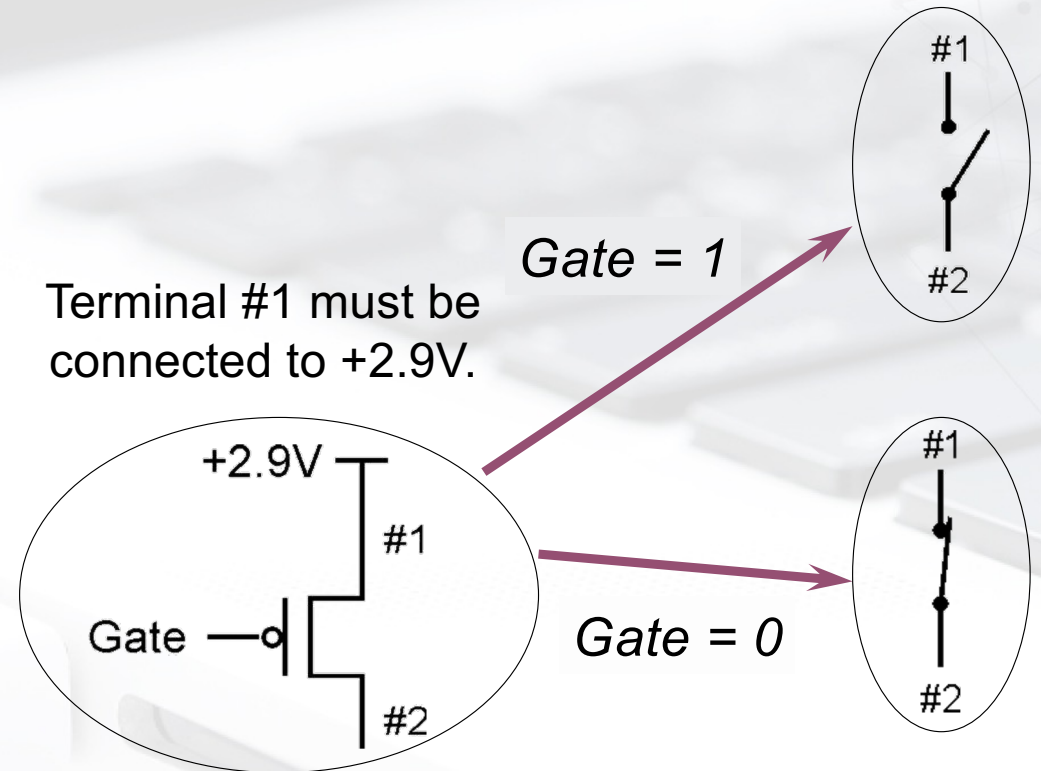

Terminal #1 must be connected to +2.9V.


Previously: Logic Gates

■ NOT vs. NOR vs. OR

 


NOT

In	Out
0	1
1	0

 

NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

 


OR

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


Previously: Logic Gates

NOT vs. NAND vs. AND

 


NOT

In	Out
0	1
1	0

 

NAND

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

 


AND

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

 Problem 3.7

■ The following circuit has a major flaw. Can you identify it?



Previously: Basic Gates

■ From Now on.....Gates


- Covered transistors mostly so that you know they exist
- Note: "Logic Gate" not related to "Gate" of transistors

■ Will study implementation in terms of gates

- Circuits that implement Boolean functions

■ More complicated gates from transistors possible

 
- XOR, Multiple-input AND-OR-Invert (AOI) gates




NOT




OR

 

NOR

 

AND

 


NAND

Previously: Logical Completeness



■ AND, OR, NOT can implement ANY truth table

INPUT			OUTPUT
A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

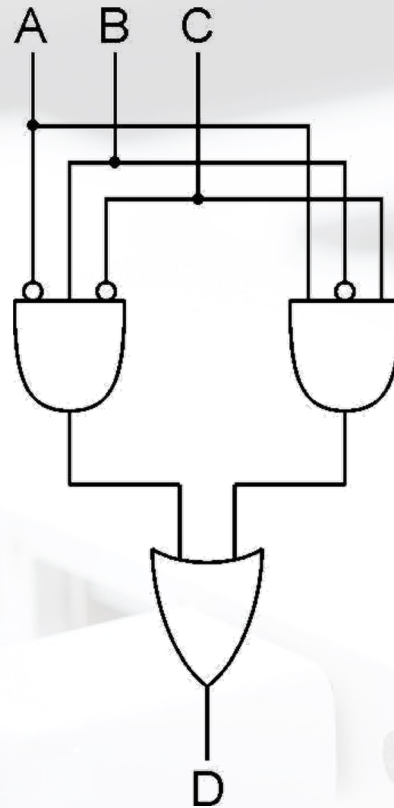


1. AND combinations that yield a "1" in the truth table.
2. OR the results of the AND gates.

Previously: Combinational Logic Circuits


■ A One-Bit Adder (aka. a Full Adder)

 - Add two bits and carry-in, produce one-bit sum and carry-out.



The truth table of a one-bit adder


A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Previously: Combinational Logic Circuits




■ Decoder

 

2-bit decoder

■ Multiplexer (MUX)

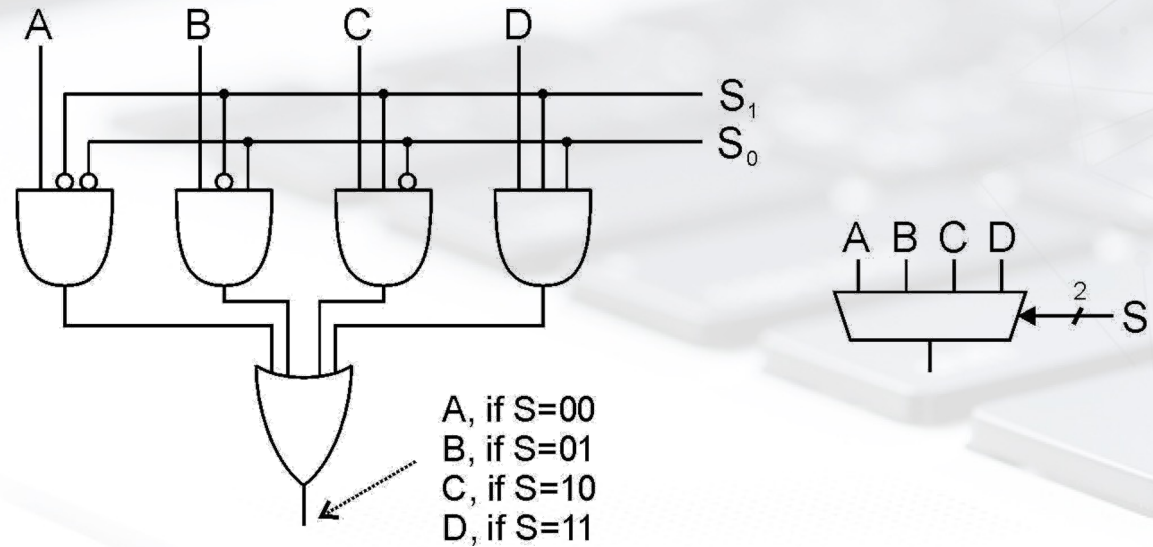


4-to-1 MUX

Previously: Basic Storage Elements




■ R-S Latch

 

S	R	out	out'
1	1	0/1	0/1
1	0	0/1	0/0
0	1	0/1	1/1
0	0	x	x

hold


■ The Gated D-Latch

 


D	WE	S	R	out
0	0	1	1	<i>hold</i>
0	1	1	0	0
1	0	1	1	<i>hold</i>
1	1	0	1	1

Previously: Basic Storage Elements

 
$(R, S) = (0, 0) \rightarrow$ Hold the previous state as $(Q_{next}, \overline{Q}_{next}) = (Q, \overline{Q})$



 $(R, S) = (1, 0) \rightarrow$ Reset as $(Q_{next}, \overline{Q}_{next}) = (0, 1)$




 $(R, S) = (0, 1) \rightarrow$ Set as $(Q_{next}, \overline{Q}_{next}) = (1, 0)$



S	R	out	out'	
0	0	0/1	0/1	<i>hold</i>
0	1	0/1	0/0	
1	0	0/1	1/1	
1	1	x	x	

 $(R, S) = (0, 1) \rightarrow$ Not allowed as $(Q_{next}, \overline{Q}_{next}) = (0, 0)$ that is not logical



Outline



1

The Transistor

2

Logic Gates

3

Combinational Logic Circuits

4

Basic Storage Elements

5

The Concept of Memory

6

Sequential Logic Circuits

7

Preview of Coming Attractions: From Logic to Data Path


Memory



■ Now that we know how to store bits, we can build a memory – a logical $k \times m$ array of stored bits.

Address Space:
number of locations
(usually a power of 2)




$k = 2^n$
locations

 


Addressability:
number of bits per location
(e.g., byte-addressable)

m bits

A $2^2 \times 3$ Memory

 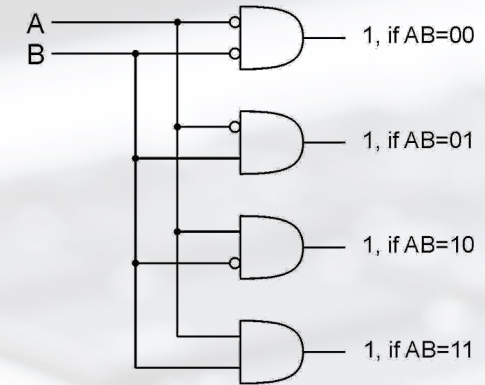 

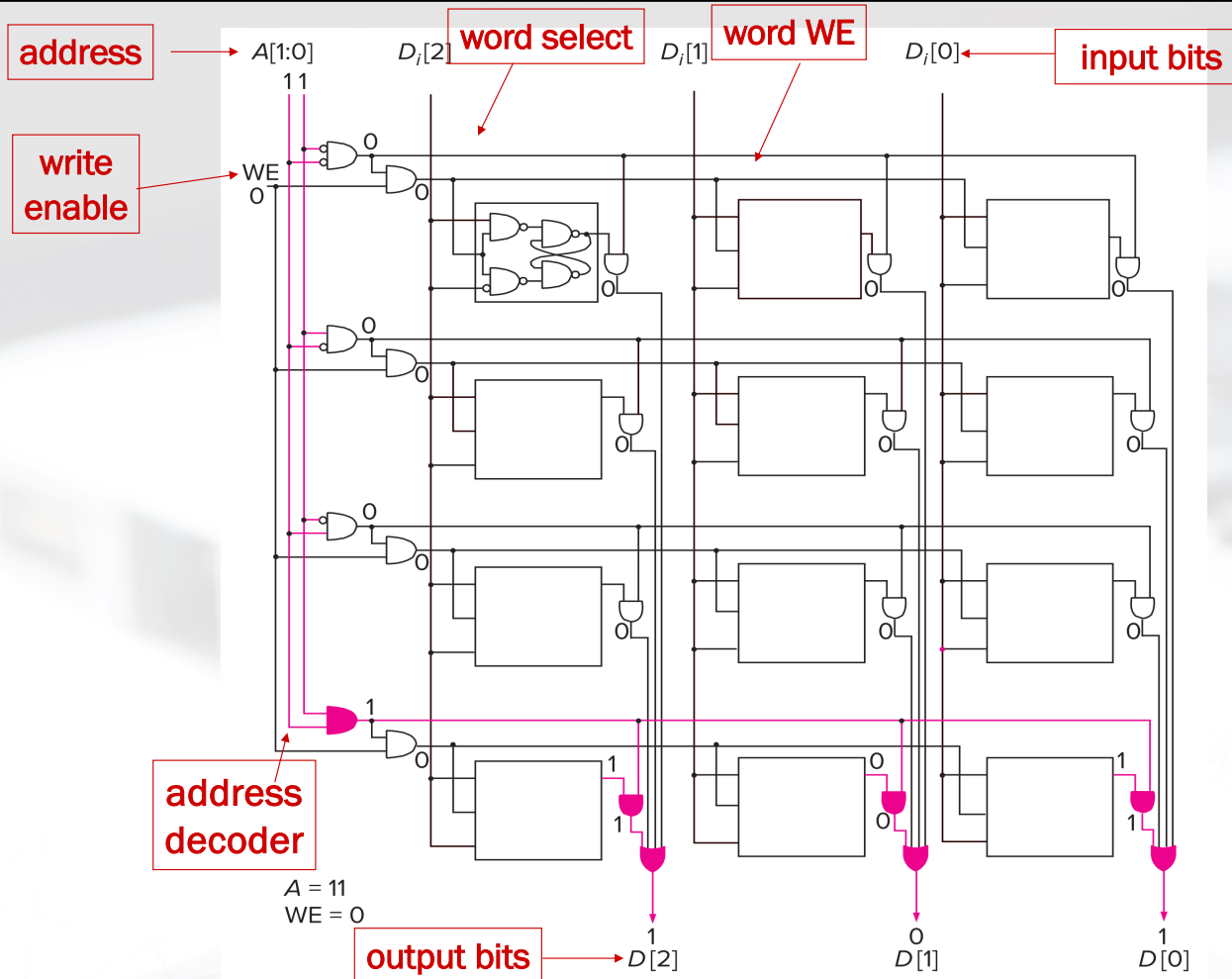Reading location 3 in our $2^2 \times 3$ memory





More Memory Details

■ This is a not the way actual memory is implemented.

- fewer transistors, much more dense, relies on electrical properties

■ But the logical structure is very similar.

- address decoder
- word select line
- word write enable

■ Two basic kinds of **RAM** (Random Access Memory)

● **Static RAM (SRAM)**

- fast, not very dense (bit-cell is a latch)

● **Dynamic RAM (DRAM)**

- slower but denser, bit storage must be periodically refreshed
- each bit-cell is a capacitor (like a leaky bucket) that decays

Also, non-volatile memories: ROM, PROM, flash, ...



More Memory Details

■ This is a not the way actual memory is implemented.

- fewer transistors, much more dense, relies on electrical properties

■ But the logical structure is very similar.

- address decoder
- word select line
- word write enable

■ Two basic kinds of **RAM** (Random Access Memory)

● **Static RAM** (SRAM)


- fast, not very dense (bit-cell is a latch)

● **Dynamic RAM** (DRAM)

- slower but denser, bit storage must be periodically refreshed
- each bit-cell is a capacitor (like a leaky bucket) that decays

Also, non-volatile memories: ROM, PROM, flash, ...

SRAM Memory

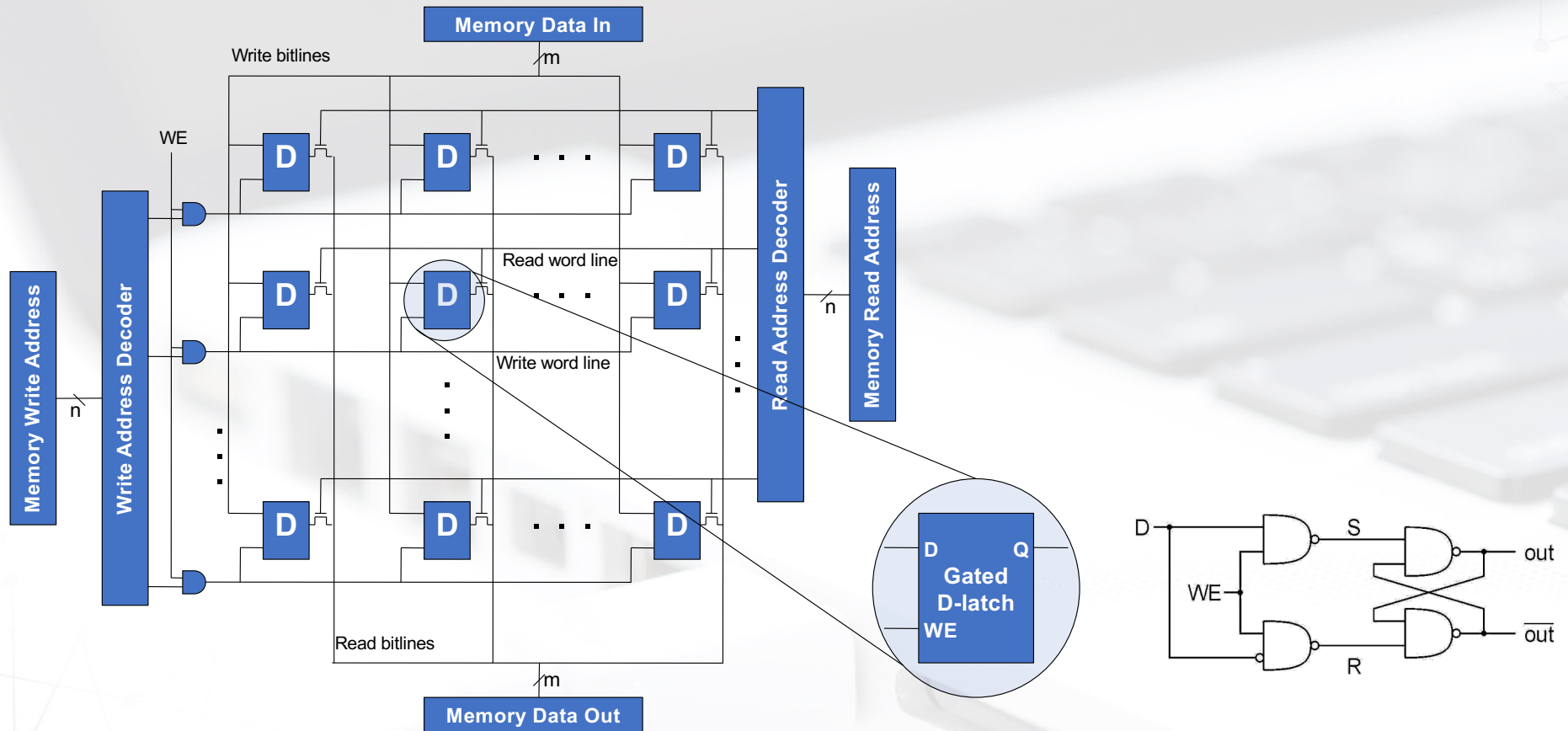



SRAM Memory



6-Transistor SRAM

3 operations

— read, write, hold

  


SRAM Memory




6-Transistor SRAM

3 operations

— read, write, hold

 

TODO : 补充读的过程

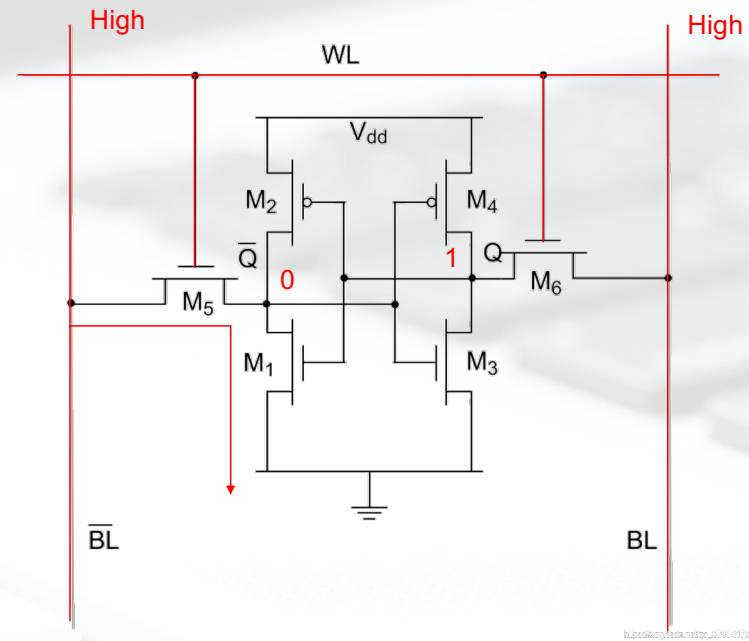



SRAM Memory



6-Transistor SRAM

3 operations




— read, write, hold

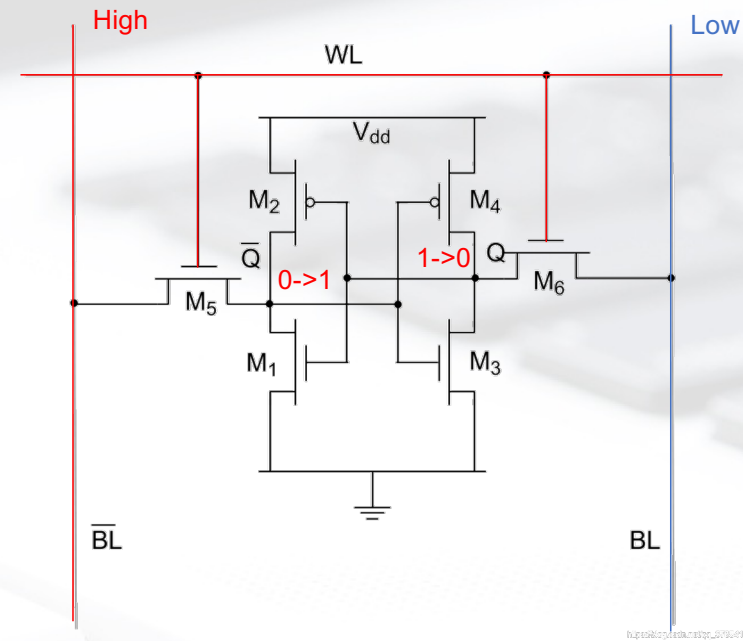 


DRAM Memory

Basic Storage Element of DRAM

   - one transistor + one capacitor
- slower but denser, bit storage must be periodically refreshed
- each bit-cell is a capacitor (like a leaky bucket) that decays



DRAM Memory

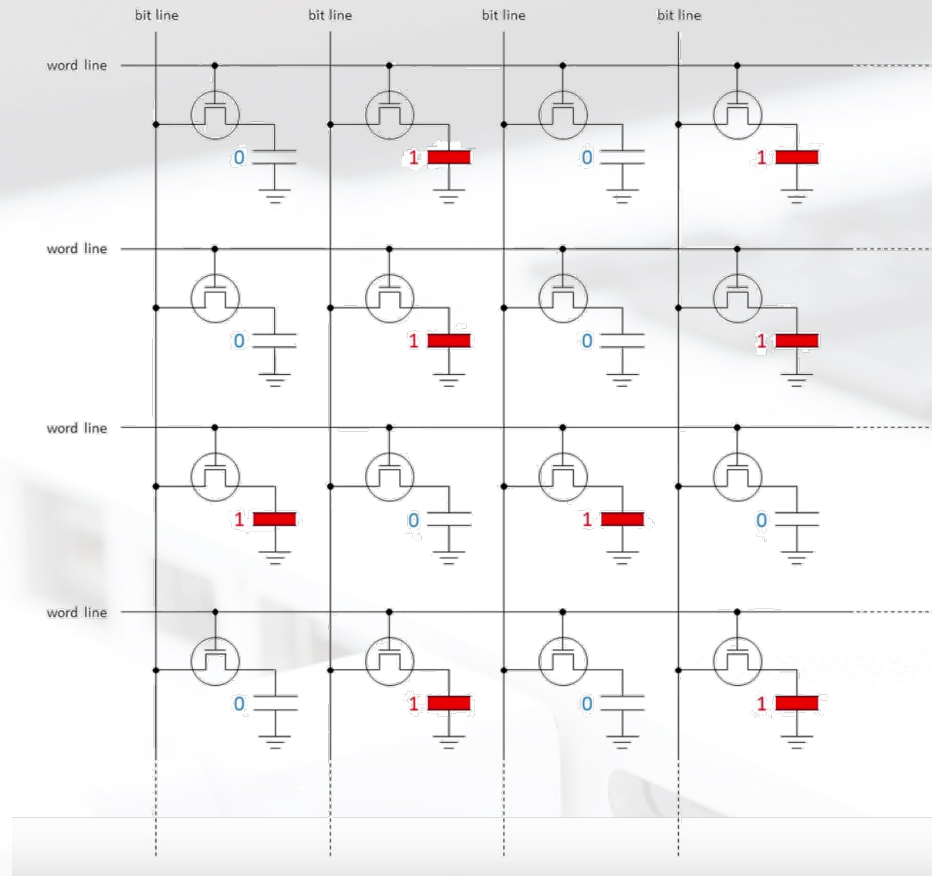


DRAM Memory



Precharge bit line


Precharge

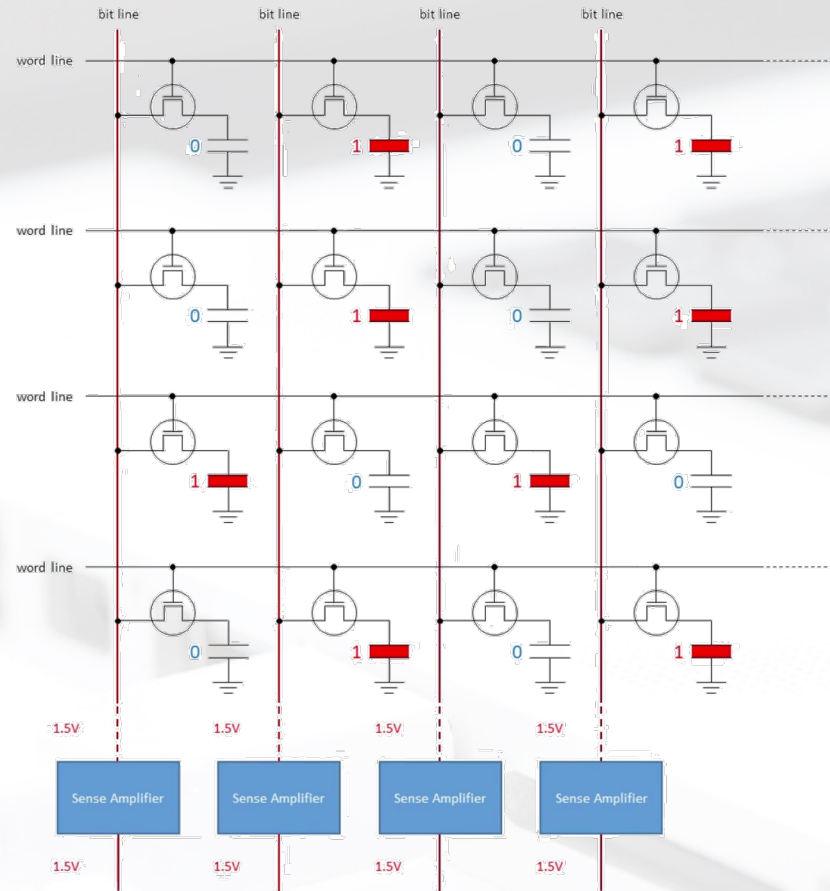

DRAM Memory



Select word line

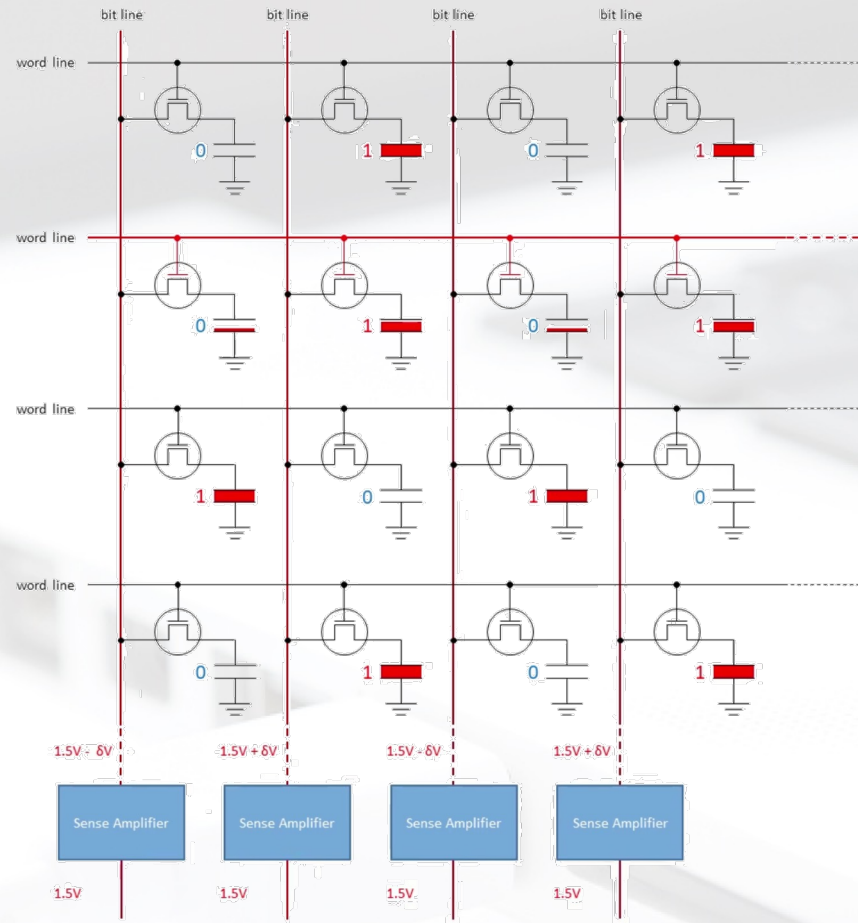


DRAM Memory



Read data with sense amplifier

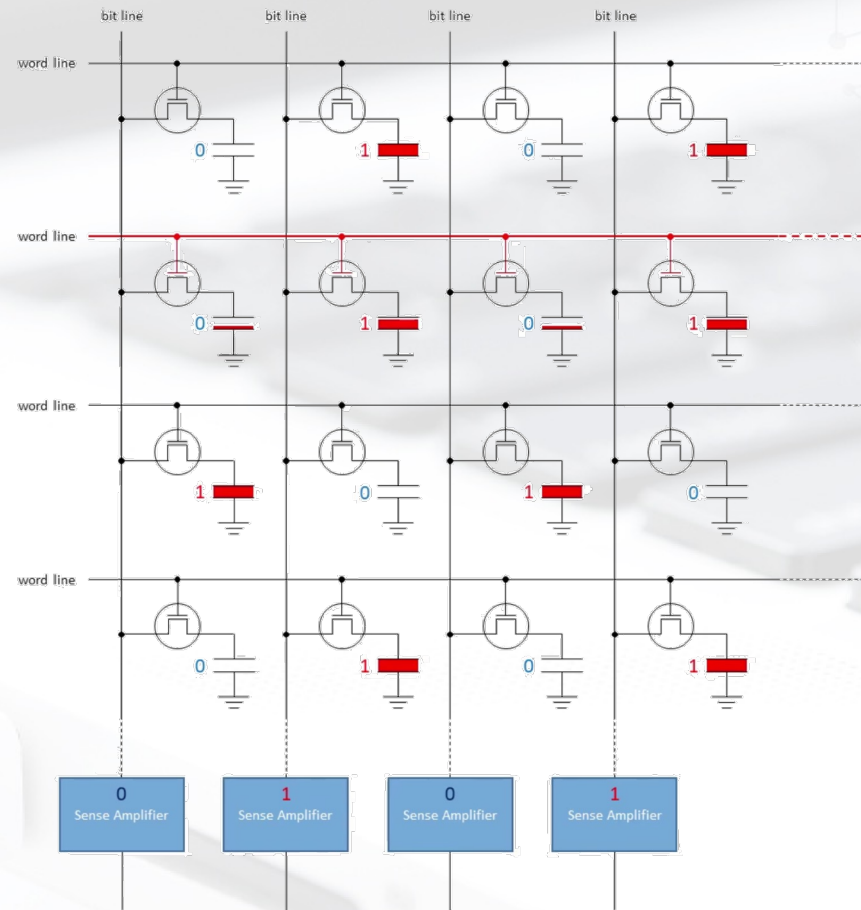- destructive read
 - when a cell is read, it must then be re-written
- Charge leakage
 - requires that all cells are periodically refreshed



Outline




- 1 The Transistor
- 2 Logic Gates
- 3 Combinational Logic Circuits
- 4 Basic Storage Elements
- 5 The Concept of Memory
- 6 Sequential Logic Circuits**
- 7 Preview of Coming Attractions: From Logic to Data Path

State Machine



Another type of sequential circuit

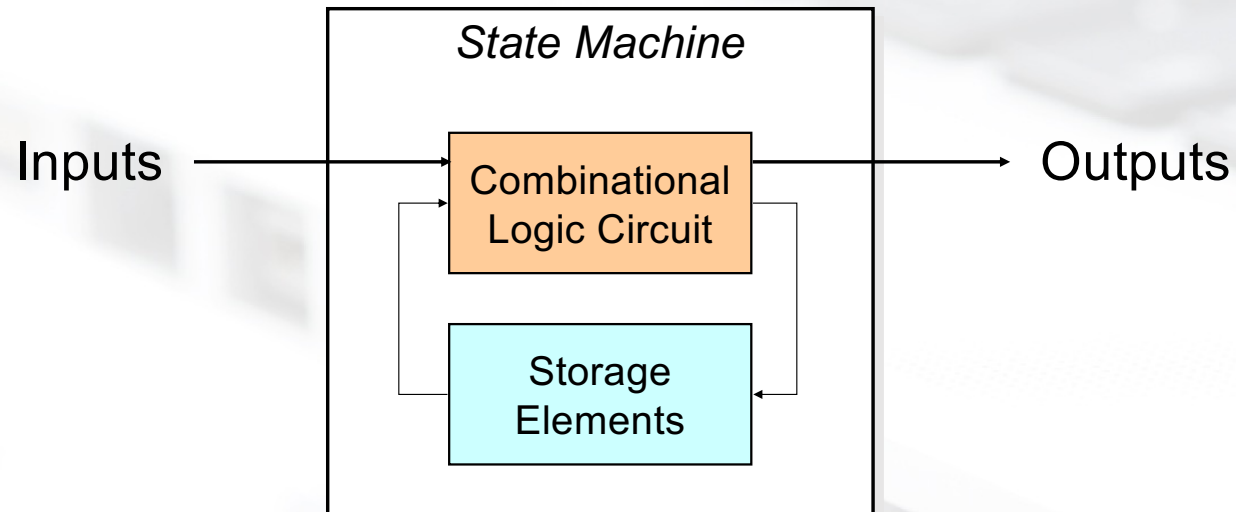
- Combines combinational logic with storage
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**




Combinational vs. Sequential



Two types of “combination” locks

 

 Combinational Lock
Success depends only on the **values**, not the order in which they are set.



Sequential Lock
Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).

State



The **state** of a system is a **snapshot of all the relevant elements** of the system at the moment the snapshot is taken.

Examples:

- The state of a basketball game can be represented by the scoreboard.

— Number of points, time remaining, possession, etc.


- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board.



State of Sequential Lock

Our lock example has four different states, labelled A-D:

 - A:** The lock is **not open**,
and no relevant operations have been performed.
- B:** The lock is **not open**,
and the user has completed the **R-13** operation.
- C:** The lock is **not open**,
and the user has completed **R-13**, followed by **L-22**.
- D:** The lock is **open**.




Sequential Lock

Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).

State Diagram of Sequential Lock



 Shows **states** and **actions** that cause a **transition** between states.




Finite State Machine



A description of a system with the following components:

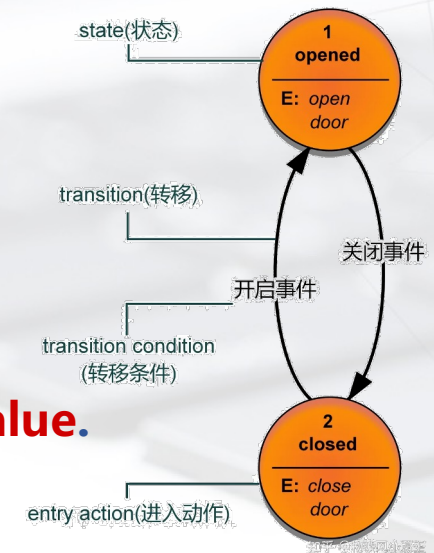1. A finite number of **states**
2. A finite number of external **inputs**
3. A finite number of external **outputs**
4. An explicit specification of all **state transitions**
5. An explicit specification of what causes each external **output value**.



Often described by **a state diagram**.

- Inputs may cause state transitions.
- Outputs are associated with each state (or with each transition).




FSM Exercise

- Even number of 0s
- Even number of 0s and even number of 1s
- Binary number dividable by 4
- String contains '110110'

FSM Example

MESI State Diagram

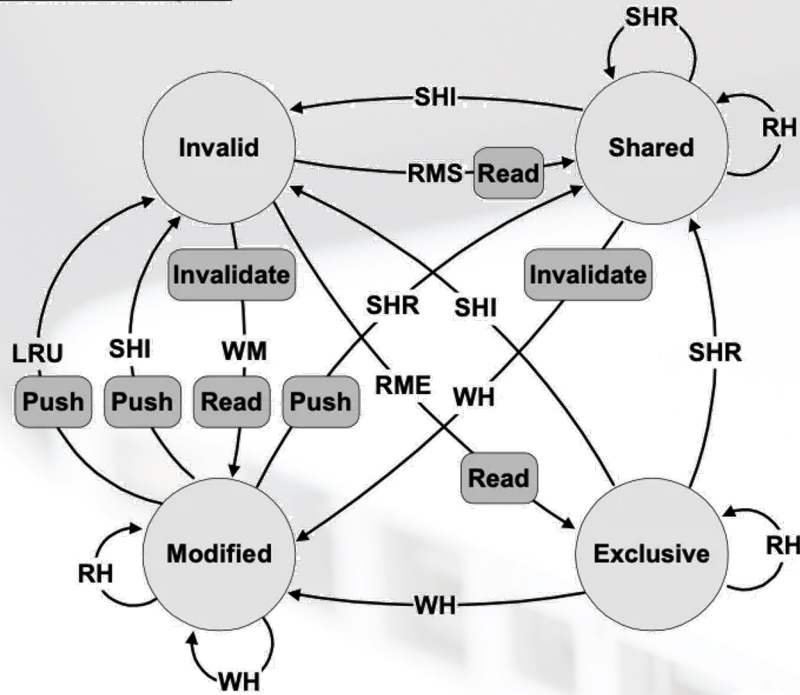


Events:

- RH = Read Hit
- RMS = Read miss, shared
- RME = Read miss, exclusive
- WH = Write hit
- WM = Write miss
- SHR = Snoop hit on read
- SHI = Snoop hit on invalidate
- LRU = LRU replacement

Bus Transactions:

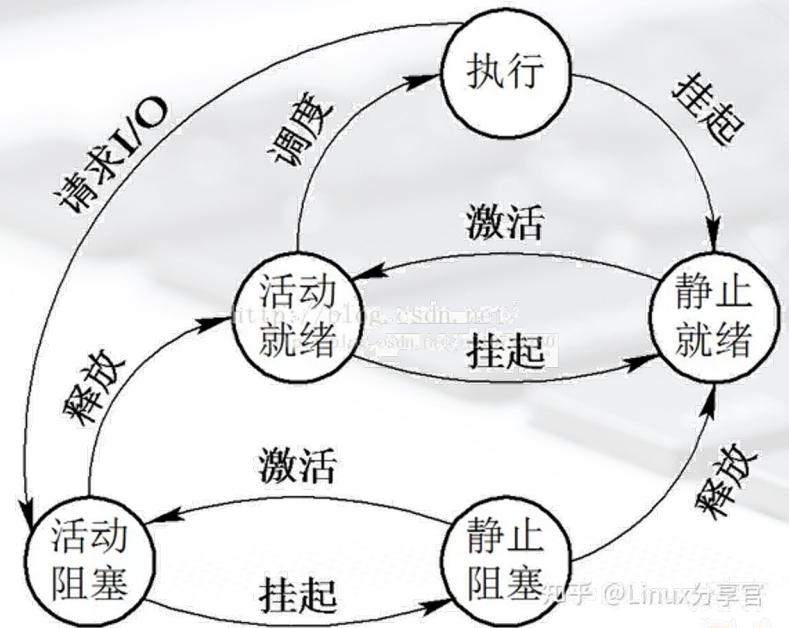- Push = Write cache line back to memory
- Invalidate = Broadcast invalidate
- Read = Read cache line from memory



Implementing a Finite State Machine




■ Combinational logic

- Determine outputs and next state.

■ Storage elements


- Maintain state representation.

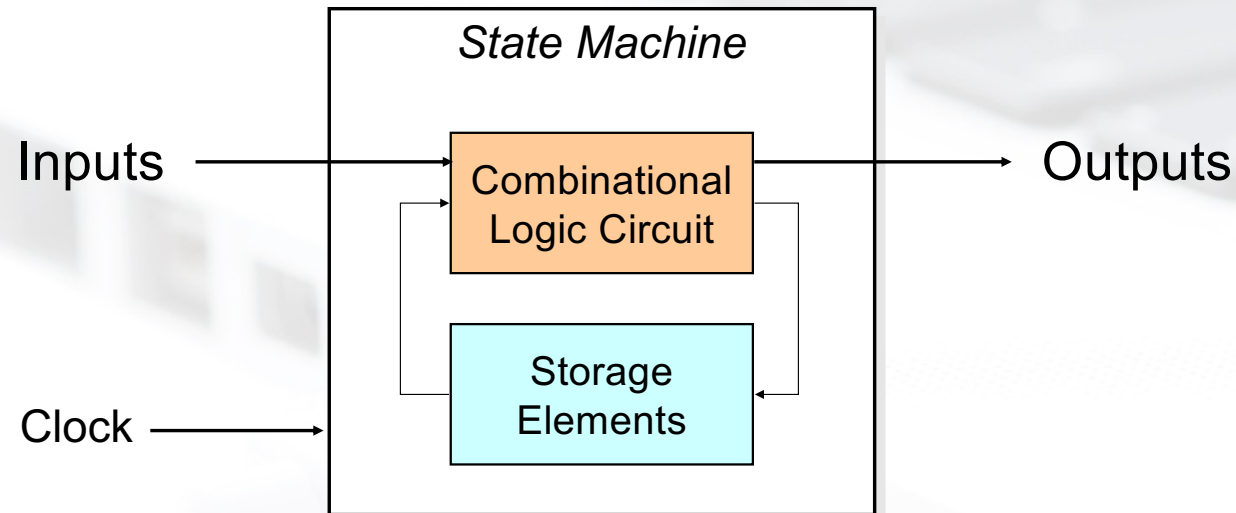

The Clock



 Frequently, a **clock circuit** triggers transition from one state to the next.




At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.

- Not always required. In lock example, the input itself triggers a transition.

Storage: Master-Slave Flipflop



 A pair of gated D-latches, to isolate *next* state from *current* state.



During 1st phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.

During 2nd phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.

Storage: Master-Slave Flipflop



A pair of gated D-latches, to isolate *next* state from *current* state.

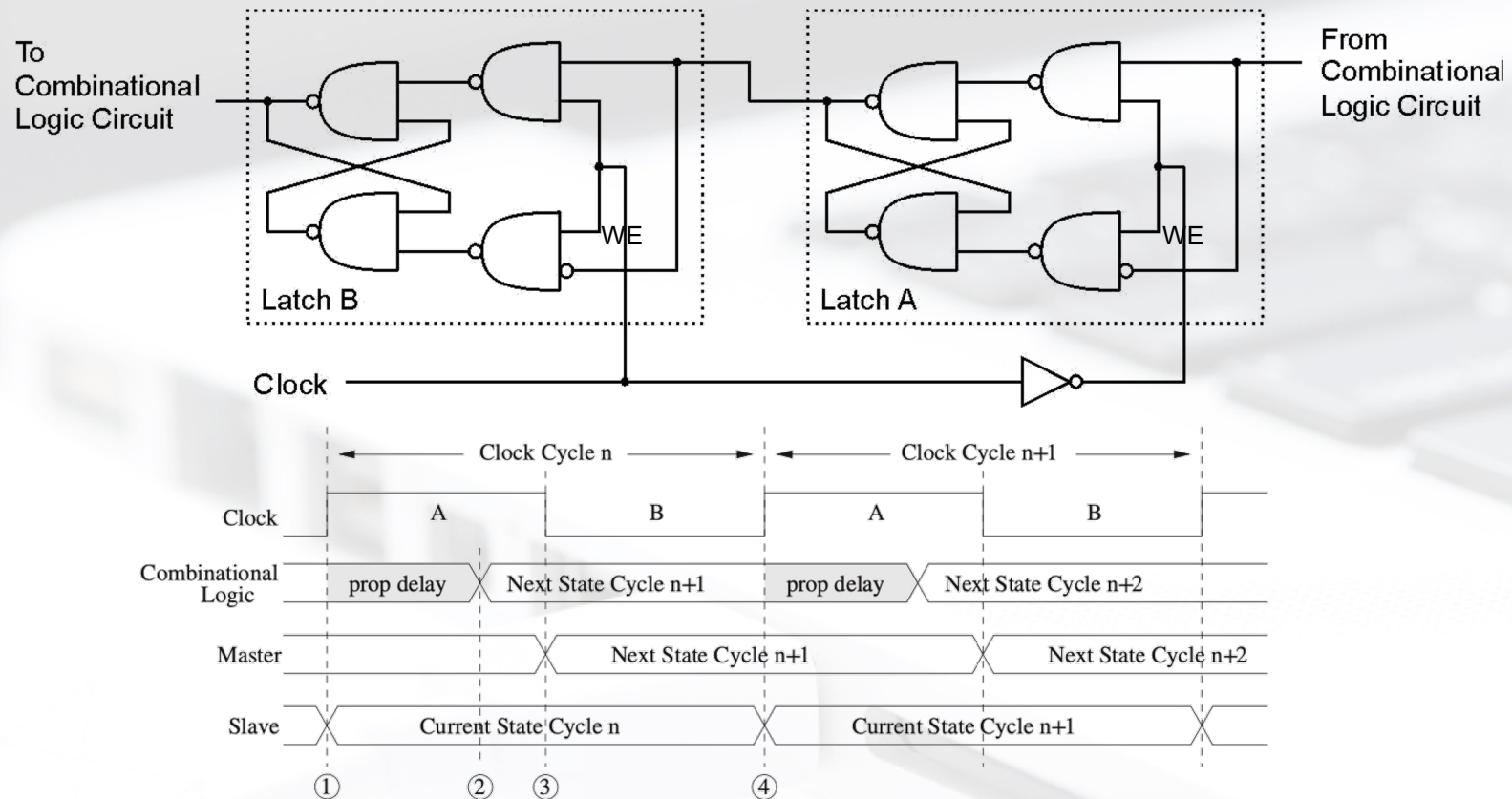


Figure 3.34 Timing diagram for a master/slave flip-flop.

Storage



Each master-slave flipflop stores one state bit.

The number of storage elements (flipflops) needed is determined by the number of states (and the representation of each state).

Examples:

- **Sequential lock**

- Four states - two bits

- **Basketball scoreboard**


- 7 bits for each score, 5 bits for minutes, 6 bits for seconds, 1 bit for possession arrow, 1 bit for half, ...

Complete Example



A blinking traffic danger sign

 - No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)




Complete Example




A blinking traffic danger sign

 - No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)




Traffic Danger Sign State Diagram

 



Transition on each clock cycle.

 Traffic Danger Sign State Diagram: State 00





Transition on each clock cycle.

  Traffic Danger Sign State Diagram: State 01





Transition on each clock cycle.

  Traffic Danger Sign State Diagram: State 10




Transition on each clock cycle.

  Traffic Danger Sign State Diagram: State 11



Transition on each clock cycle.

 Traffic Danger Sign State Diagram: State 00



Transition on each clock cycle.

Traffic Danger Sign Truth Tables



Outputs
(depend only on state: S_1S_0)

S_1	S_0	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1

Lights 1 and 2
Lights 3 and 4
Light 5



Next State: $S_1'S_0'$
(depend on state and input)

In	S_1	S_0	S_1'	S_0'
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Switch

Whenever $In=0$, next state is 00.

Traffic Danger Sign Logic

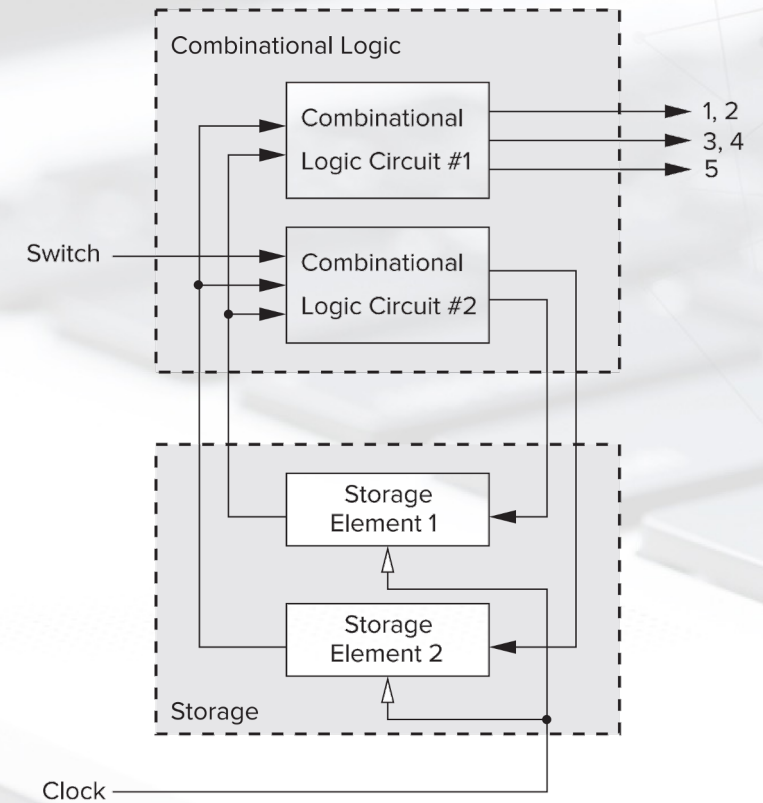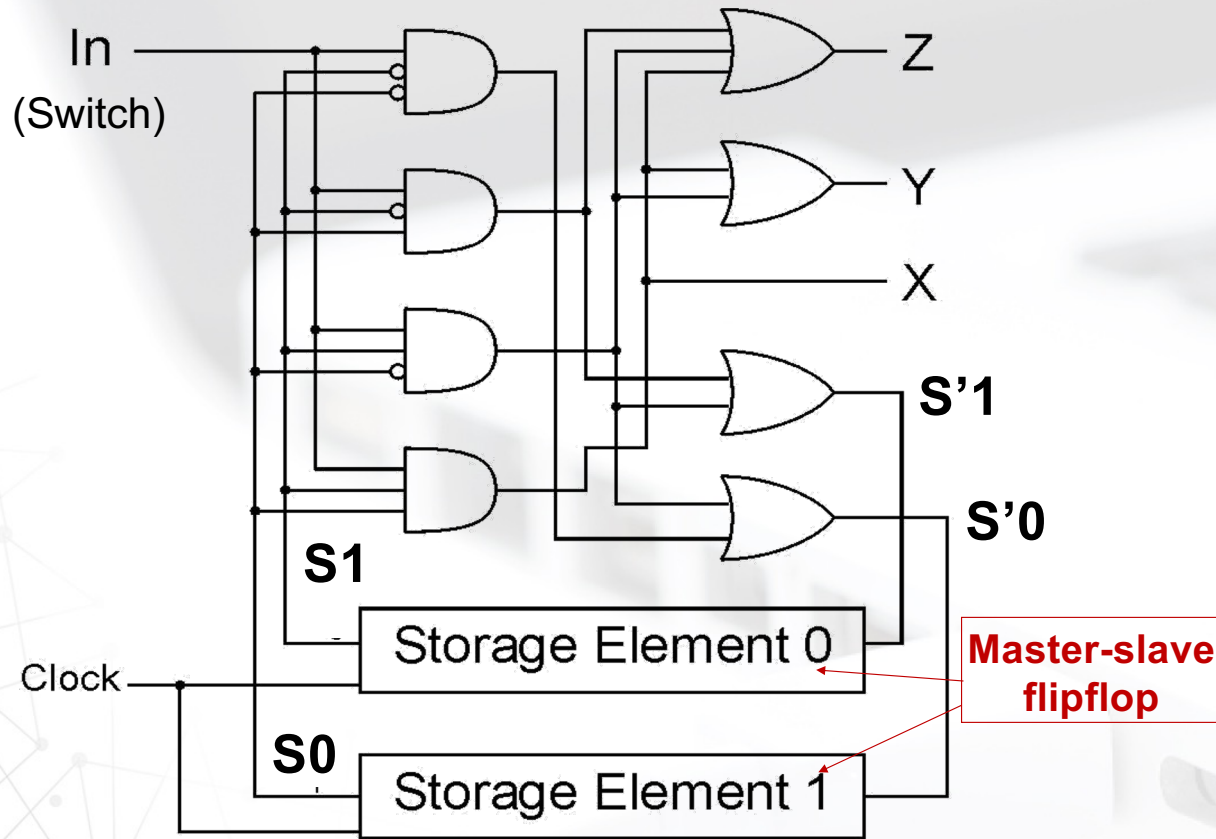

Outline



- 1 The Transistor
- 2 Logic Gates
- 3 Combinational Logic Circuits
- 4 Basic Storage Elements
- 5 The Concept of Memory
- 6 Sequential Logic Circuits
- 7 Preview of Coming Attractions: From Logic to Data Path**



From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-3 on next slide.


Combinational Logic

- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

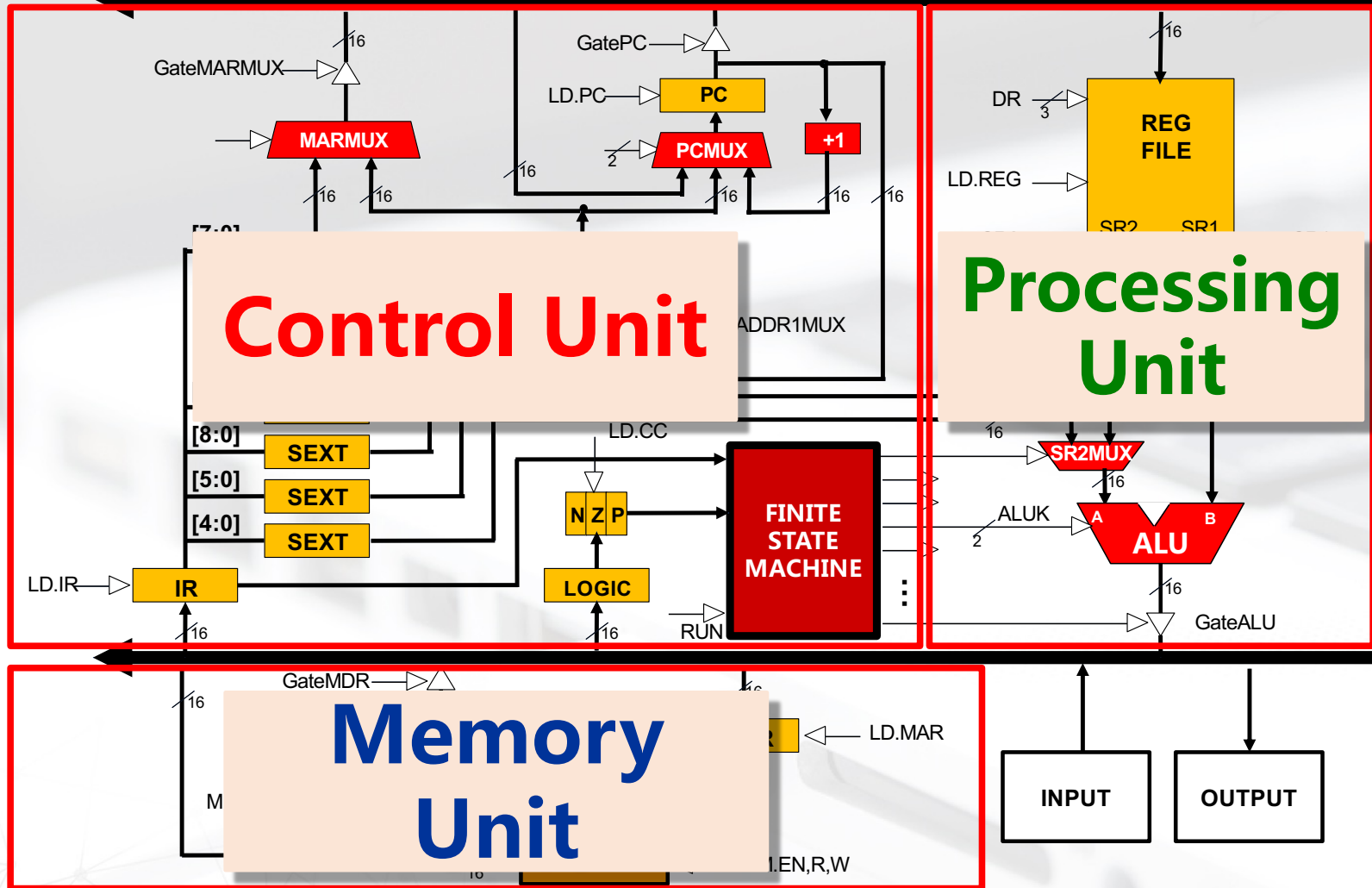LC-3 Data Path Overview (Microarchitecture)





Register



■ A register stores a multi-bit value.

  - We use a collection of D-latches, all controlled by a common WE.
- When $WE=1$, n-bit value D is written to register.



■ A four-bit register

- We use a collection of flip-flops instead of D-latches
- Read the contents of a register throughout a clock cycle
- And store a new value in the register at the end of that same clock cycle

 


Figure 3.36 A four-bit register.

Summary



■ We' ve touched on basic digital logic

- Transistors
- Gates
- Storage (latches, flip-flops, memory)
- State machines

■ Built some simple circuits

- adder, subtracter, adder/subtracter, Incrementer
- Counter (consisting of register and incrementer)
- Hard-coded traffic sign state machine
- Programmable traffic sign state machine

■ Up next: a computer as a (simple?) state machine

LC-3 Data Path

